



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Power-Supply Circuits](#) > APP 1071

Keywords: charge pump, charge-pump doubler, negative supply, digital-to-analog converter , DAC, voltage output DAC, sensor bias, LCD contrast bias, voltage-controlled oscillator, VCO

APPLICATION NOTE 1071

DAC-Powered Charge Pump Varies Negative Rail

Jul 09, 1998

Abstract: This application note presents an adjustable negative supply that uses an inverting-doubler charge pump controlled by an 8-bit, serial-input, digital-to-analog converter (DAC). This circuit with a negative supply rail is suitable for as a sensor bias, LCD contrast bias, or voltage-controlled oscillator (VCO) tuning supply.

A related idea appeared in the July 21, 1997 issue of *Electronic Design*.

The circuit shown in **Figure 1** provides a low-current, adjustable negative supply rail suitable for use as a sensor bias, liquid-crystal-display (LCD) contrast bias, or voltage-controlled-oscillator (VCO) tuning supply. By operating a charge-pump doubler from the output of a buffered digital-to-analog converter (DAC), the circuit avoids the customary approach involving clumsy level shifters based on op amps and discrete components.

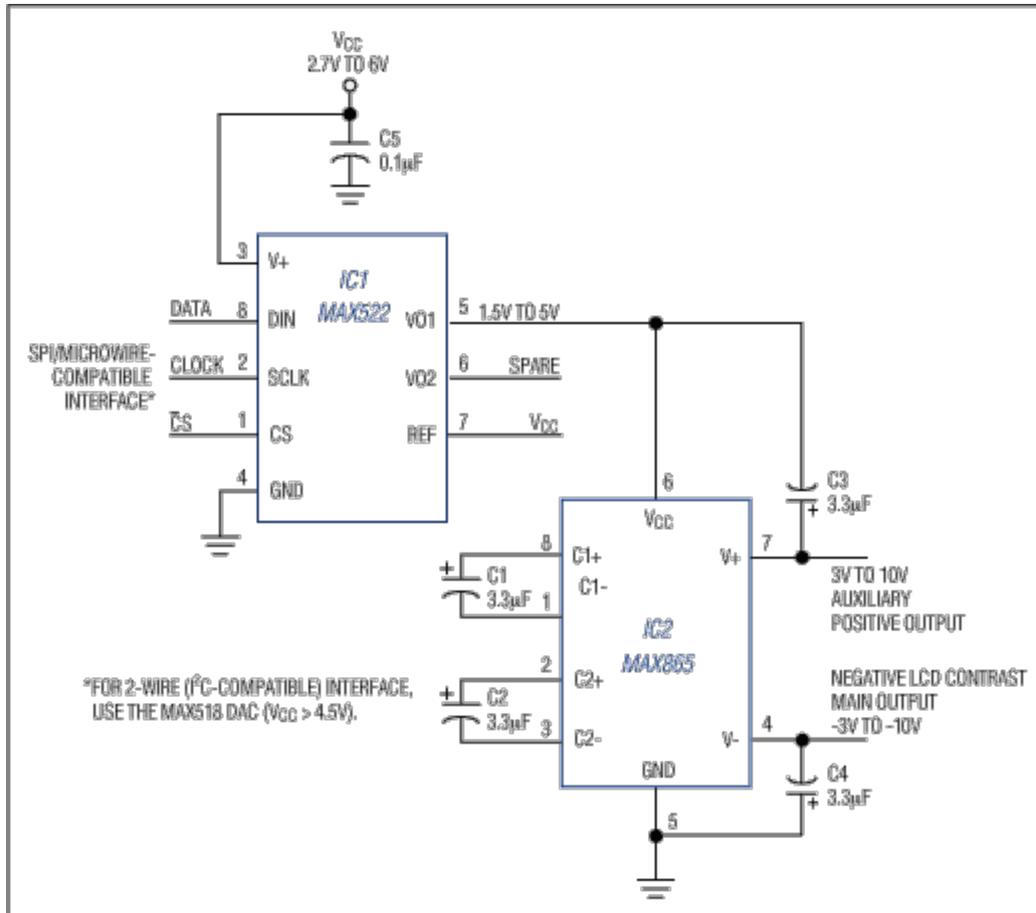


Figure 1. This adjustable negative supply consists of an inverting-doubler charge pump controlled by an 8-bit, serial-input DAC.

IC1 is a dual, 8-bit DAC with serial input and buffered voltage outputs. Output impedances are 50Ω; therefore, the DAC output in use drops about 50mV while providing the 1.1mA typically drawn by the IC2 charge pump. As the input code varies from 0 to 255, the DAC output ranges rail-to-rail, changing approximately 40mV per step.

With a +5V input (V_{CC}) applied to IC1 and a -3V output from IC2, the code that produces the minimum allowable voltage to the charge pump (1.5V) is 80 (decimal). The charge pump draws 0.6mA and generates ±2 times the voltage at its V_{CC} terminal, producing ±3V to ±12V as its input ranges from 1.5V to 6V. (The positive and negative outputs can be used simultaneously.) The main power can go as low as 2.7V, producing a negative output slightly over -5V. The minimum code for this condition is about 140 (decimal).

To shut down the supply, simply write zeros to the DAC. The DAC itself has a shutdown mode that draws only 1μA. To ensure a reliable start-up when bringing the system out of shutdown, write a value that powers the charge pump with a minimum of 2V. Note that a microcontroller (μC) with a pulse-width-modulation (PWM) output can eliminate the DAC altogether. For example, you can provide a variable V_{CC} to the charge pump by filtering a 20kHz PWM signal with a 270Ω/3.3μF lowpass network. Be sure the μC's port pin can supply the current with an acceptable voltage drop; if not, buffer it with a CMOS buffer or inverter such as the 74HC04.

Related Parts

MAX522	Dual, 8-Bit, Voltage-Output Serial DAC in 8-Pin SO Package	Free Samples
MAX552	+3V/+5V, 12-Bit, Serial, Multiplying DACs in 10-Pin μ MAX Package	Free Samples
MAX865	Compact, Dual-Output Charge Pump	Free Samples

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 1071: <http://www.maximintegrated.com/an1071>

APPLICATION NOTE 1071, AN1071, AN 1071, APP1071, Appnote1071, Appnote 1071

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>