

Maxim > Design Support > Technical Documents > Application Notes > Wireless and RF > APP 4286

Keywords: MAX2659, GPS, LNA, low band rejection

APPLICATION NOTE 4286

Providing Additional Low-Frequency Rejection with the MAX2659 GSP Low-Noise Amplifier (LNA)

By: Roger Bremer, Strategic Applications Engineer Sep 22, 2008

Abstract: This application note explains how to achieve additional immunity to GPS and cellular band signals when GPS is included in a wireless handset. Additional low-frequency rejection can be added to the design by altering the MAX2659 low-noise amplifier's (LNA) input match. The article explains how to adjust the LNA topology, and advises what performance tradeoffs to expect.

GPS receivers are increasingly included in wireless handsets. This colocation with the handset's transmitter can present a strong jamming signal at the LNA input in the GSP path. It is possible to achieve additional immunity to GSM and cellular band signals, if the MAX2659 low-noise amplifier (LNA) is used in the design. One simply needs to alter the LNA's input match from the standard match referenced in the data sheet. By adding one additional component, the input match can be changed from a lowpass topology to a highpass topology to knock down the GSM or cellular signals. The extra low-band rejection provided by the new match comes at a tradeoff of gain and noise figure.



components used in a typical radio transceiver.

The matching network listed below offers an additional 10dB of attenuation at the upper end of the E-GSM-900 band. The noise figure only degrades by 0.1dB and gain decreases by 0.3dB.



			915MHz Suppression Relative to In-Band (dB)	849MHz Suppression Relative to In-Band (dB)
Standard	20.5	0.8	11.6	13.3
Highpass	20.2	0.9	21.6	25.0

Related Parts		
MAX2659	GPS/GNSS Low-Noise Amplifier	Free Samples

More Information

For Technical Support: http://www.maximintegrated.com/support For Samples: http://www.maximintegrated.com/samples Other Questions and Comments: http://www.maximintegrated.com/contact

Application Note 4286: http://www.maximintegrated.com/an4286 APPLICATION NOTE 4286, AN4286, AN 4286, APP4286, Appnote4286, Appnote 4286 Copyright © by Maxim Integrated Products Additional Legal Notices: http://www.maximintegrated.com/legal