Keywords: current limited, current-limit, switch, digital potentiometer, digital pots, P channel switch, switches

APPLICATION NOTE 298

Current-Limit Switch Is Digitally Programmable

Aug 17, 2000

Abstract: Current-limit switches are virtually ubiquitous in system controls. They provide a safe means for regulating the current delivered to a load circuit. The switches allow the load current to increase to a programmed limit but no higher. This application note illustrates the implementation of a digitally programmable current-limit switch using MAX890L a current-limited, high-side P-channel switch and MAX5160 digital potentiometer

Additional Information:
- Quick View Data Sheet for the MAX1983
- Quick View Data Sheet for the MAX5160
- Technical Support: Power

Current-limit switches are virtually ubiquitous in system controls. They provide a safe means for regulating the current delivered to a load circuit. The switches allow the load current to increase to a programmed limit but no higher. Typically, the current limit is a function of the voltage across an external resistor, produced by the current from a fixed source internal to the switch IC. This voltage serves as the reference for an internal current-limiting amplifier. By replacing the resistor with a digital potentiometer, you can easily program the current limit (see the figure below). IC_1 is a current-limit switch with a maximum programmable limit of 1A. The limit equals $1380/R_{SET}$, where R_{SET} is the resistance between pins 5 and 6 of IC_2. IC_2 is a 50kΩ digital potentiometer whose resistance is programmable in 32 equal increments. With active-low CS held low, high-to-low transitions at active-low INC(pin 1) increments IC_2's internal counter.
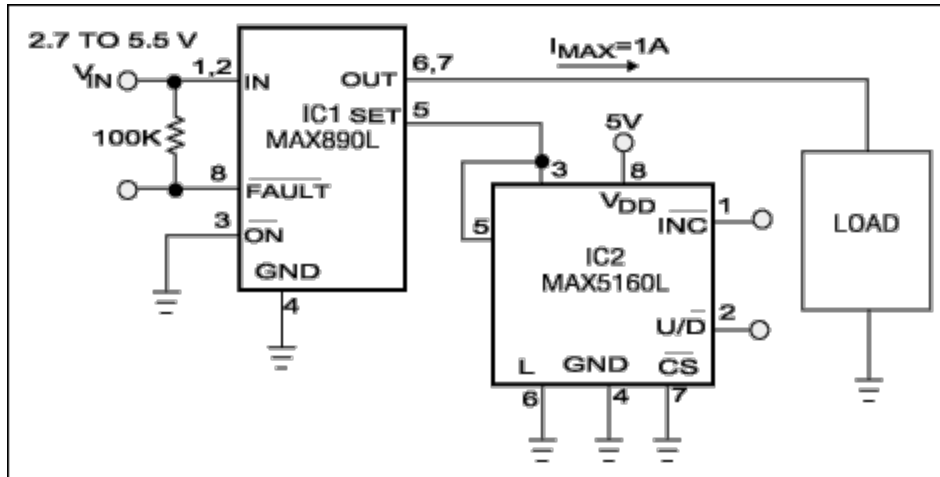
Figure 1. You can program a current limit to 1A in 32 equal increments by using a digital potentiometer.

These transitions increase the resistance between W and L when U/active-low D is low and reduce it when U/active-low D is high. IC_1 includes a thermal-shutdown capability that turns the load current completely off when the chip temperature exceeds 135°C. It restores the load current when the temperature cools by 10°C. If the short-circuit fault is still present, the switch cycles off and on, yielding a pulsed load current. An open-drain fault output (pin 8) switches low when the load demands current beyond the programmed limit, enabling an external system to monitor the condition of the current switch.

A similar version of this article appeared in the August 17, 2000 issue of *EDN*.

Related Parts		
MAX5160	Low-Power Digital Potentiometers	Free Samples
MAX890L	1.2A, Current-Limited, High-Side P-Channel Switch with Thermal Shutdown	Free Samples

More Information
For Technical Support: http://www.maximintegrated.com/support
For Samples: http://www.maximintegrated.com/samples
Other Questions and Comments: http://www.maximintegrated.com/contact

Application Note 298: http://www.maximintegrated.com/an298
APPLICATION NOTE 298, AN298, AN 298, APP298, Appnote298, Appnote 298
Copyright © by Maxim Integrated Products
Additional Legal Notices: http://www.maximintegrated.com/legal